

The Good, The Bad and The Ugly

ACØC Alpha 76pa

One Man's Modernization
- or Unforgivable Butchering -
of a Classic Workhorse Amp

Jeff Blaine – ACØC

Presented to the KC DX Club – 27 June 2011

Beginnings: The Good

It's not your SB200...

- Functional on all bands
- Power output within expected limits
- Great reliability history
- Fit on the bench slot
- Ceramic tube complement
- Reasonably quiet fan

Beginnings: The Bad

Rode hard and put away wet

- Intermittent power out under some cases
- Clunky open-frame TR relay
- Transformer hum under load (common for the EI)
- Unobtainium tube type (8874)
- No grid drive protection
- 120V PTT switching input

Beginnings: The Ugly

Rode hard and put away wet (paint)

- Alpha's famous non-drying paint
- Incandescent functional but dim lighting


The Mods

Mod: New Faceplate + Screws




Mod: Case Prep and Painting

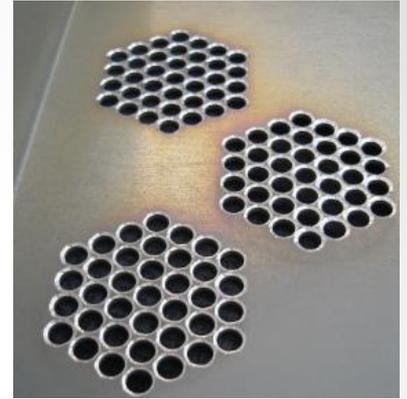- Interior tube vents were chamfered to improve flow
- Case roughed, degreased and painted with plastic matte-finish paint



Mod: LED for Meter Illumination

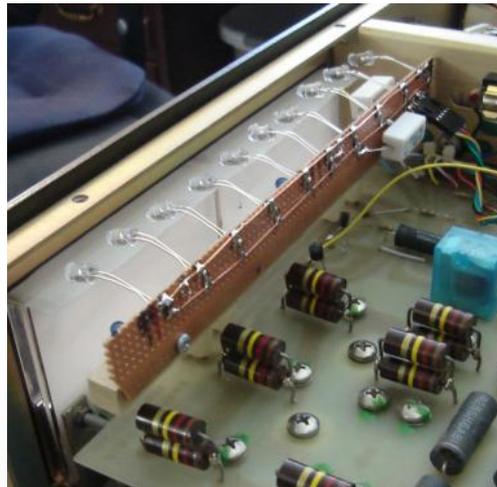- Stock incandessent lamps replaced with a string of white and blue LEDs
- The board is temporary mounted and ties into existing control circuit




Mod: Plate Choke Swap

- Stock choke is resonant on the 12m band
- Replaced with an Ameritron unit with added turns




Mod: Coupling Cap Swap

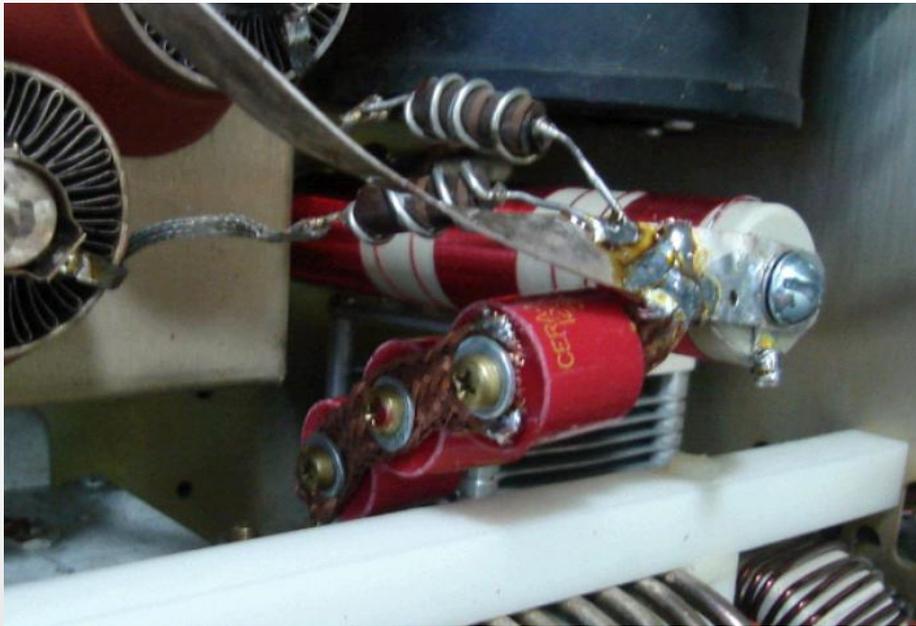- Replaced stock ceramic with TV type door knobs
- Coupling caps are one of the heating spots observed with the SB200 mod




Mod: TR Relay Swap

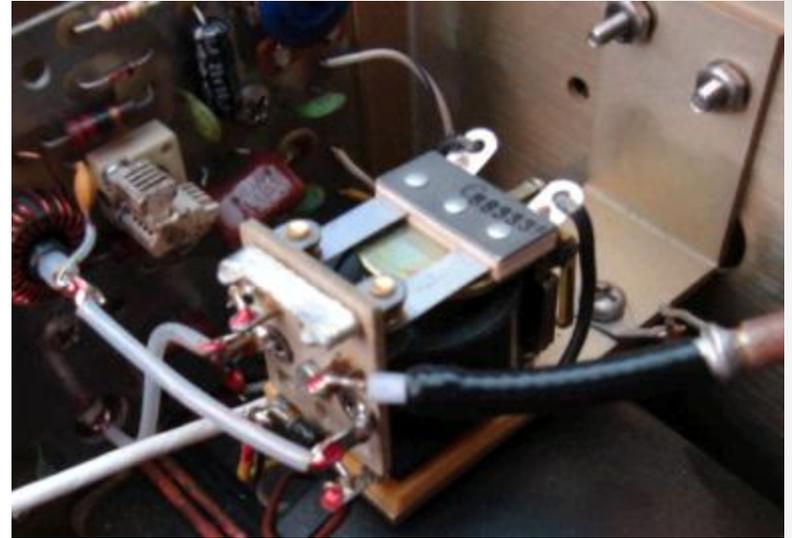- Stock open frame swap with Panasonic RF reed input relay + GV vac output relay
- Sound deadning:
 1. Foam mounted
 2. Braid connected
 3. Hot glue



Mod: Replacing the Missing Solder

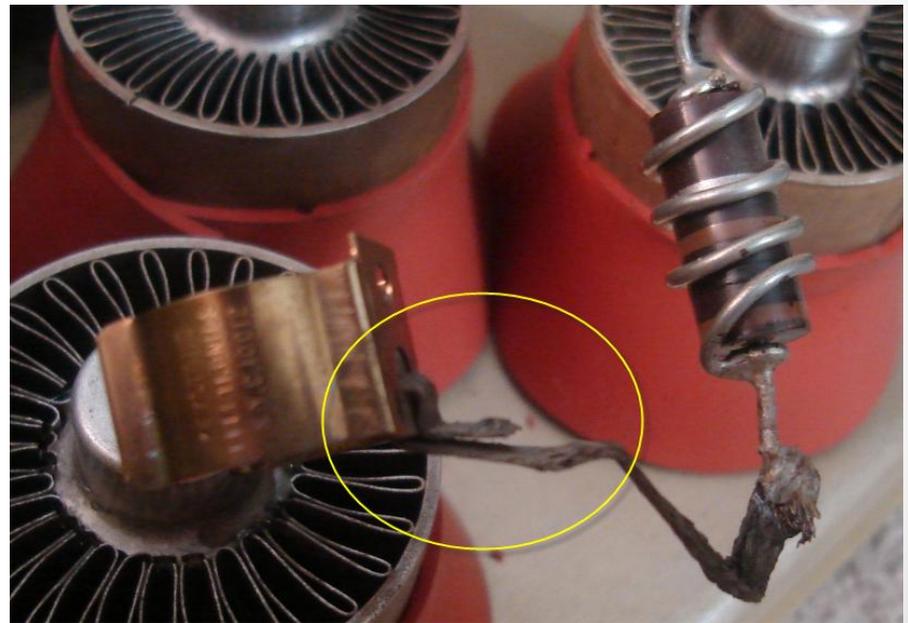- Solder braid on tube clamps and on bandswitch had serious solder voids
- The tube cap opens were easy to find... the bandswitch intermittent opens were not




What about the Grid Protection?

- Amp has overcurrent protection
- SWR limit provided by external LP100 + PTT line
- Grid protection capability needed

Considering the K6XX Solution

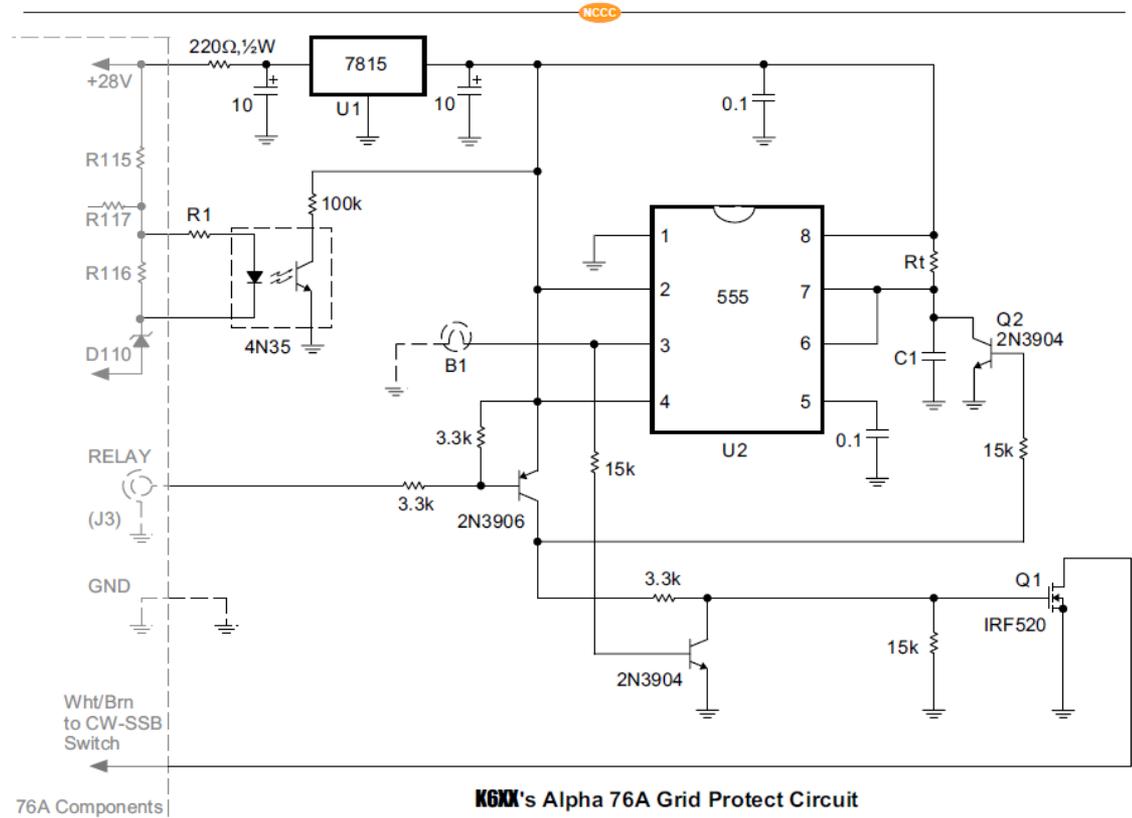- Uses voltage across existing resistor + opto iso as current source to trigger a timer
- Problems:
Ckt errors and lack of warning level



A uP Alternative

- The opto iso sampling method for the grid current is really an elegant idea
- Stick same sensor onto the ADC of a uP, and could read grid current directly
- The uP also opens the door to a lot of cool features including QSK, relay sequencing, temp monitoring, fan speed control, others. Oh my...

uP Control Board

Functional Overview

- Real-time grid current measurement - warning and lockout
- 3 mS QSK switching speeds with rig inhibit output
- Automatic fan speed control - based on tube and transformer temperatures
- 4x20 LCD display on a remotely mounted control head
- Real-time measurement of tube and transformer temps - peak-hold function to indicate the max temps reached
- Standby function
- Morse code beeps provide audio clues for key events

uP Control Board Operation Summary


- Inputs:

- Grid current sense
- PTT from transmitter
- Tube temp sensor
- TX temp sensor
- Amp power ON
- AC line sensor
- Reflected power sense


- Outputs:

- Bias line
- TR relay
- LCD
- LED
- TX inhibit
- Speaker


Control Board Topology

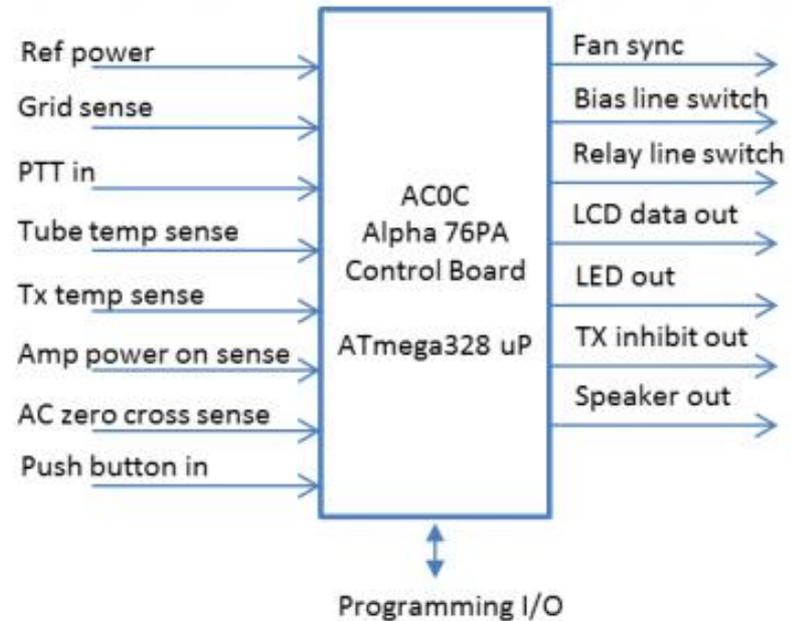


Schematic – Page 1

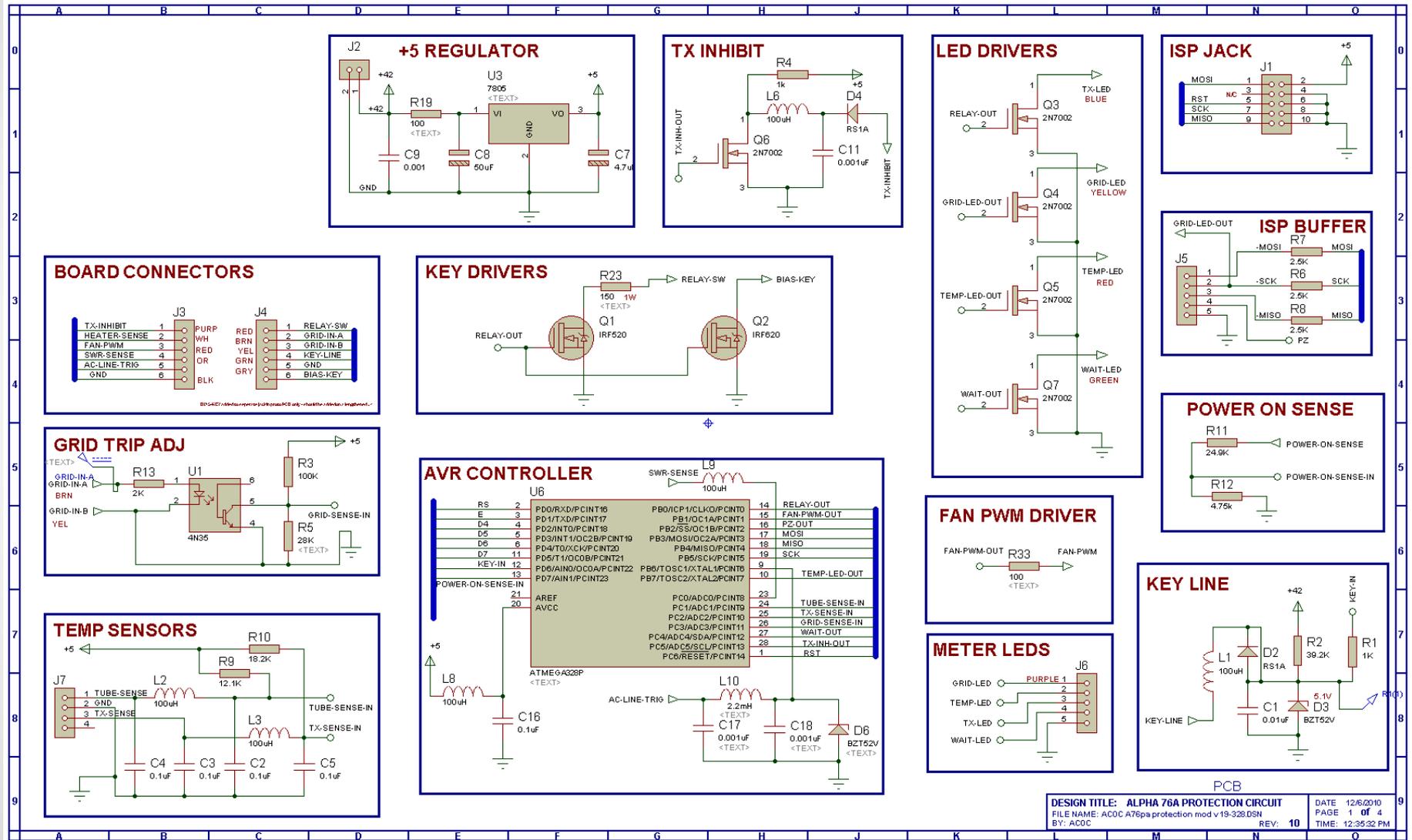

Schematic – Page 2

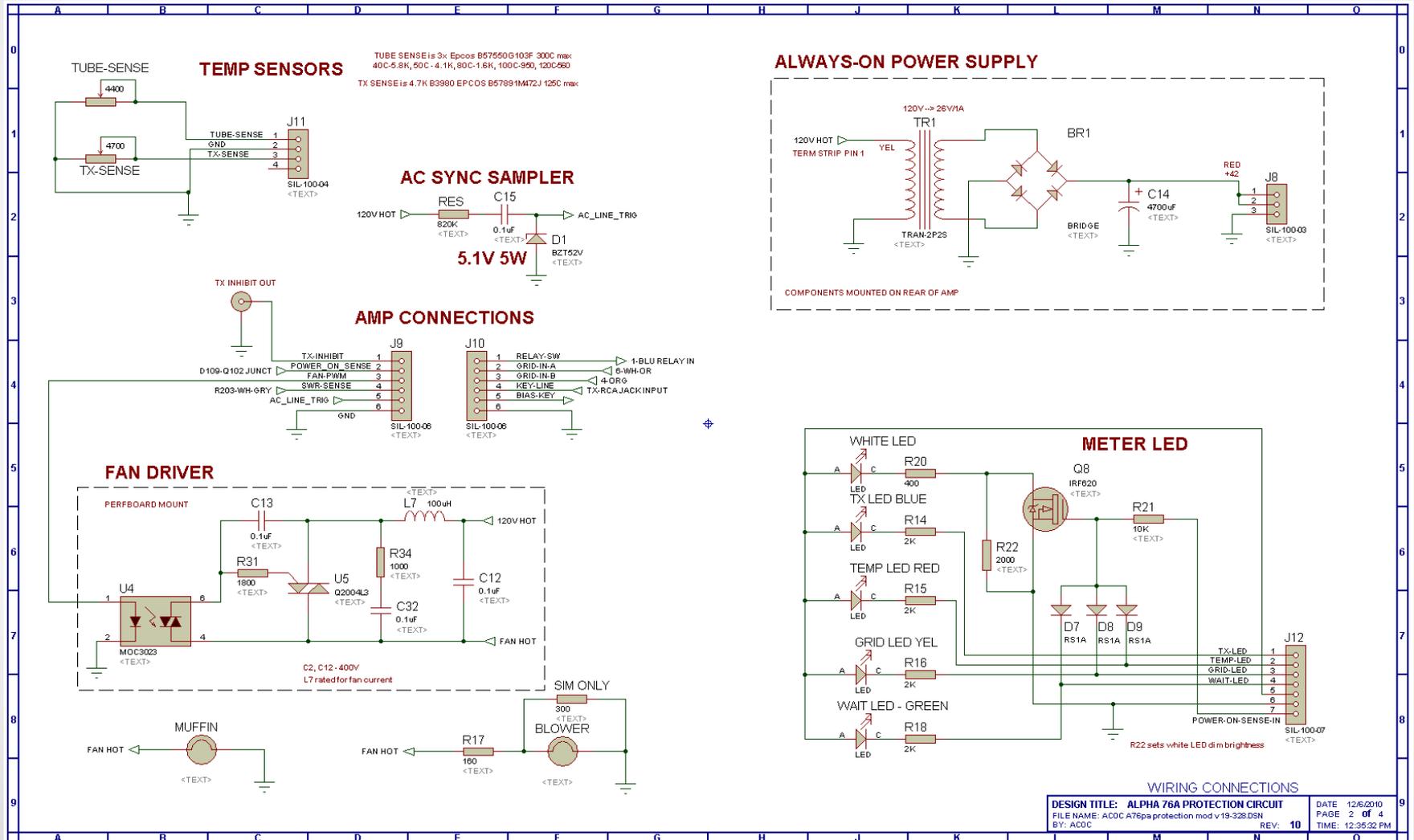

Schematic – Page 3

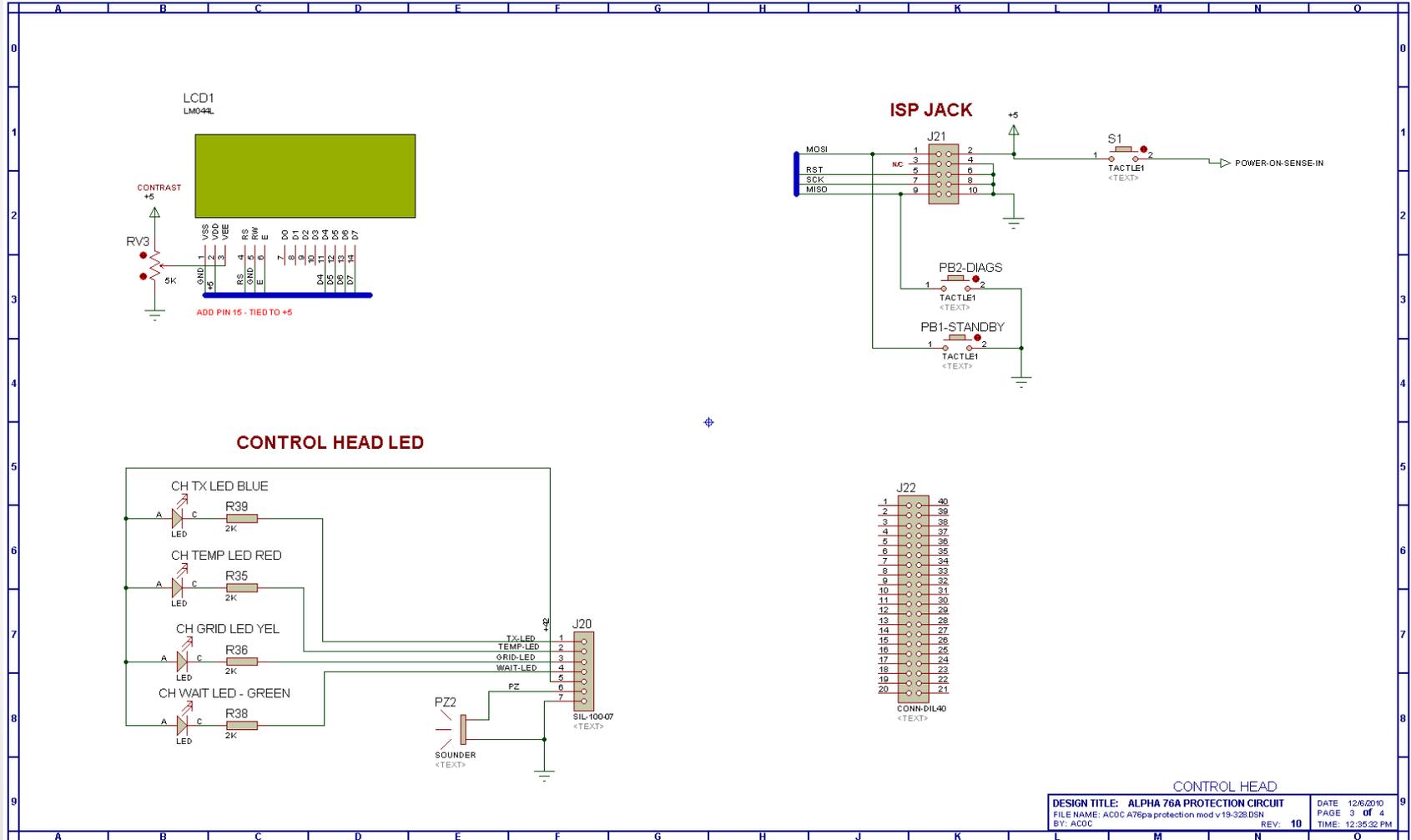


CONTROL HEAD





DESIGN TITLE: ALPHA 76A PROTECTION CIRCUIT	DATE: 12/6/2010
FILE NAME: ACOC A76pa protection mod v19-328.DSN	PAGE: 3 of 4
BY: ACOC	REV: 10
	TIME: 12:35:32 PM

uP Control Board


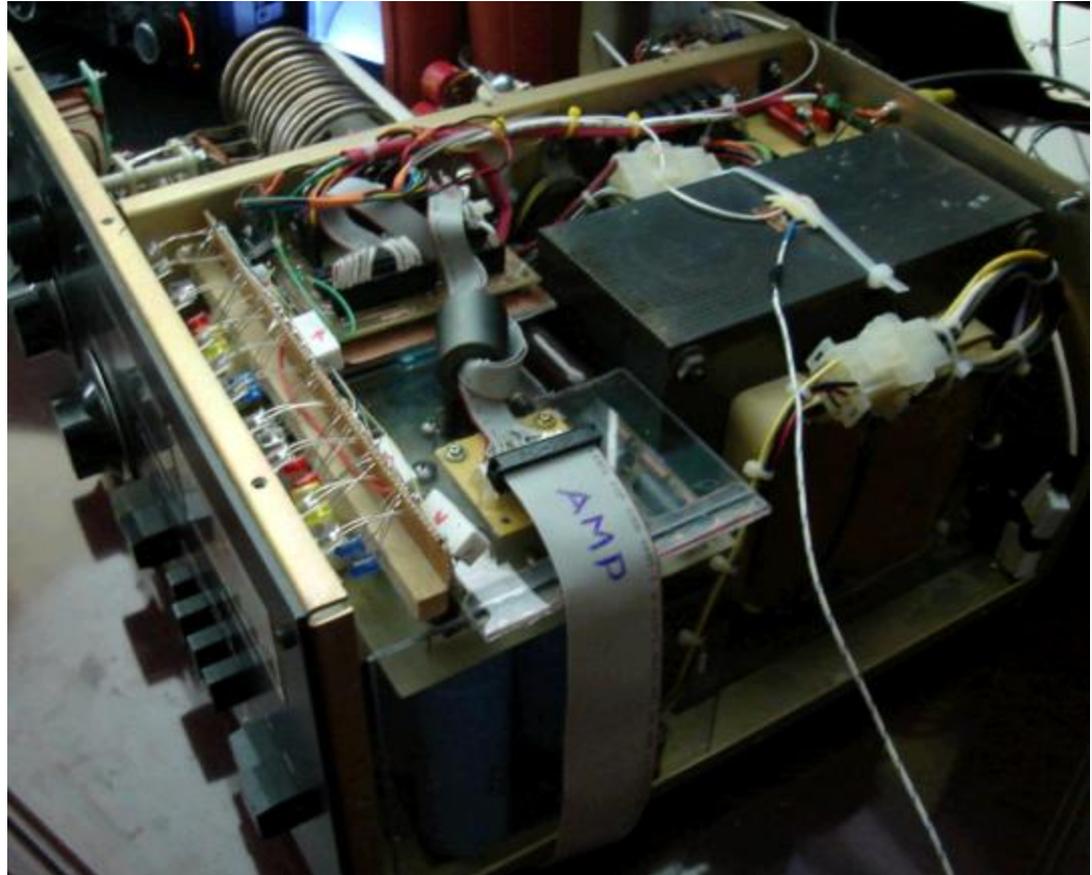
- Fit into amp sitting over the power supply and control board



uP Control Board - Mounting

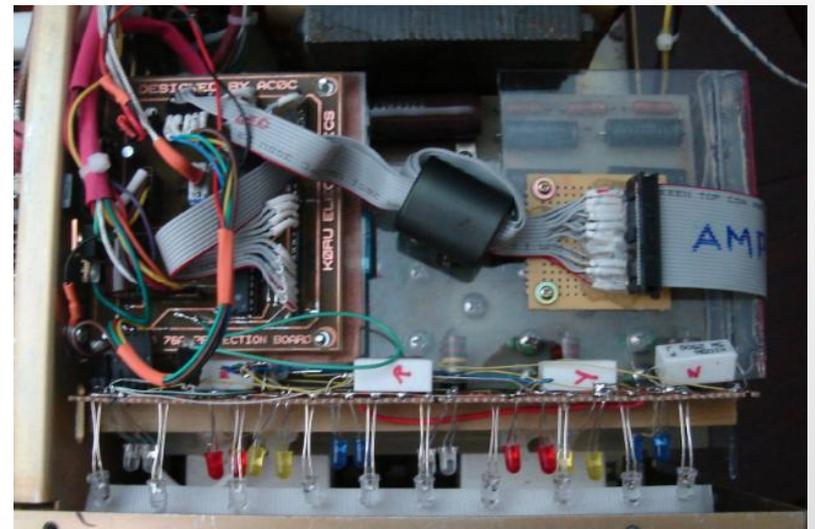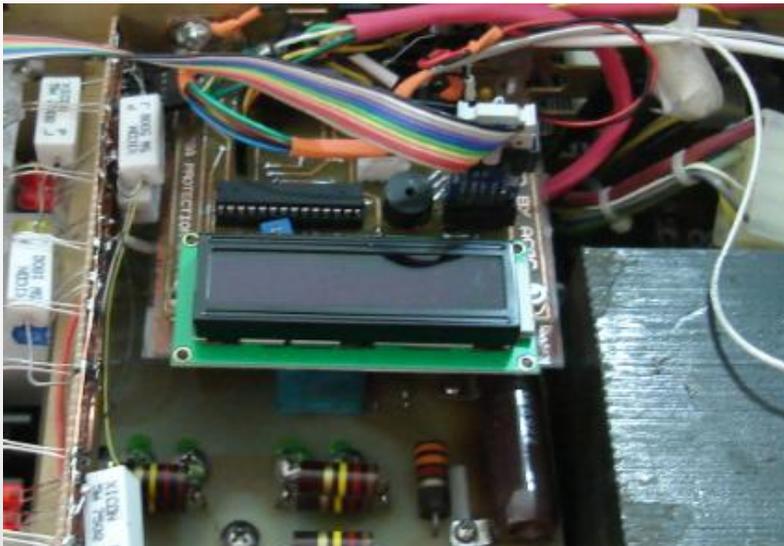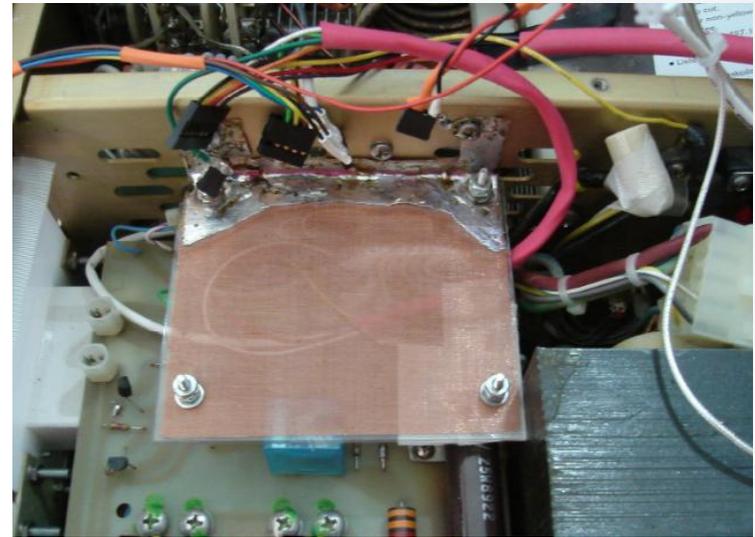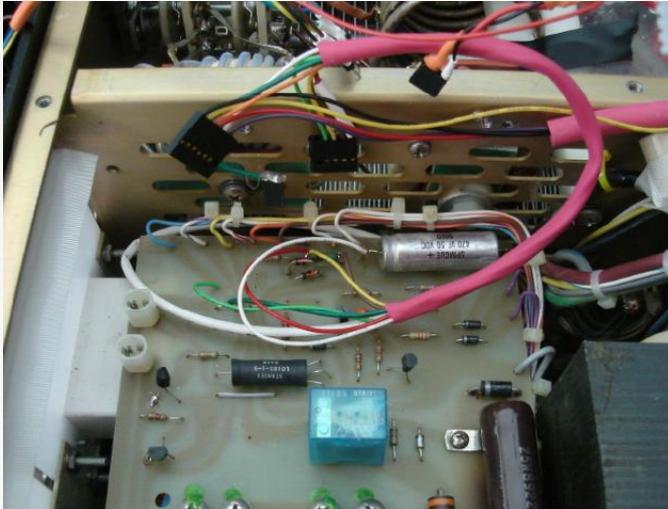


uP Control Board – Temp Sensors

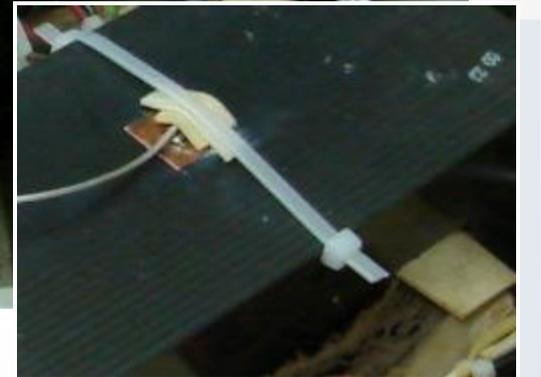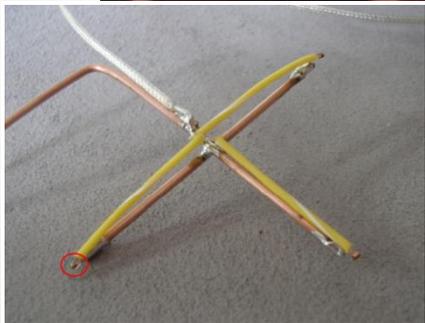



uP Control – Fan System

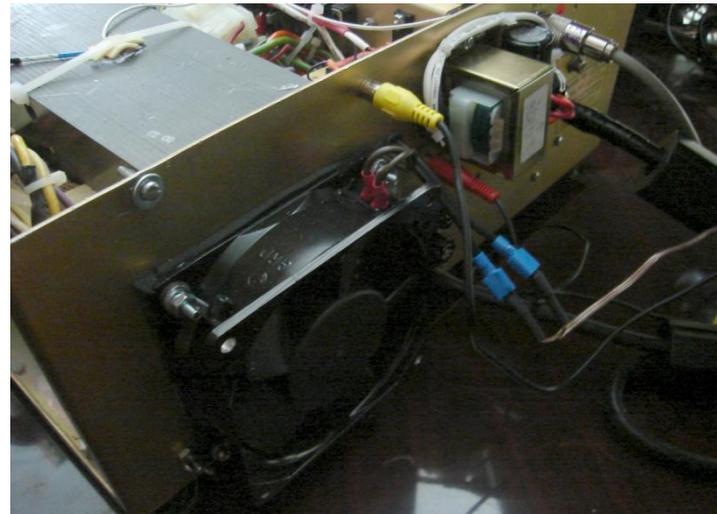- uP controls internal blower, rear-mounted muffin and desk mounted muffin above the amp
- Fan speed determined by tube and transformer temps





uP Control Board Construction

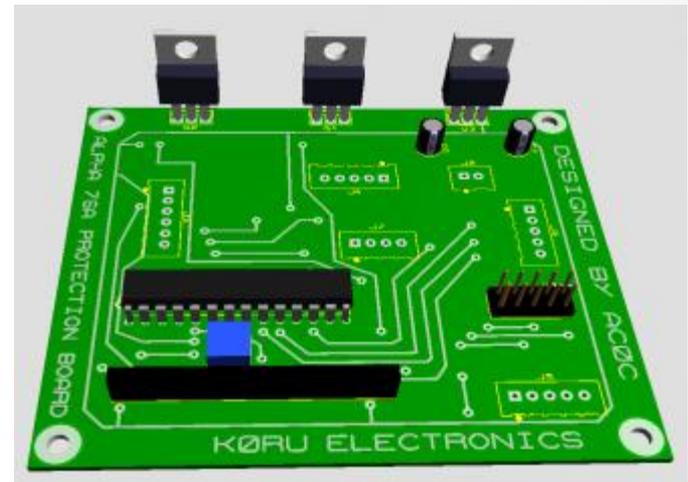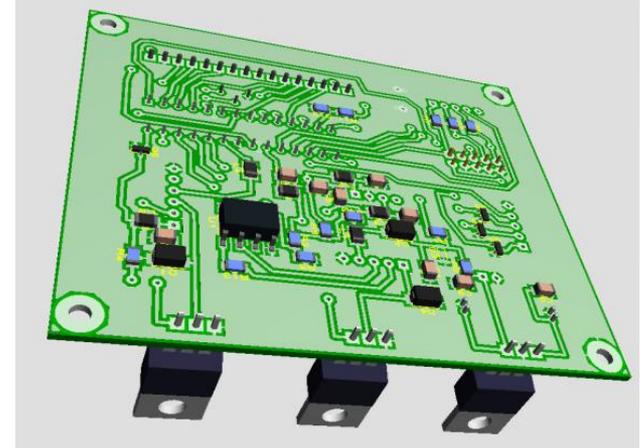- PCB by KORU
- Double sided SMT construction
- Size of space available and connections were a challenge



uP External Control Head

- Control head sits on shelf above amp

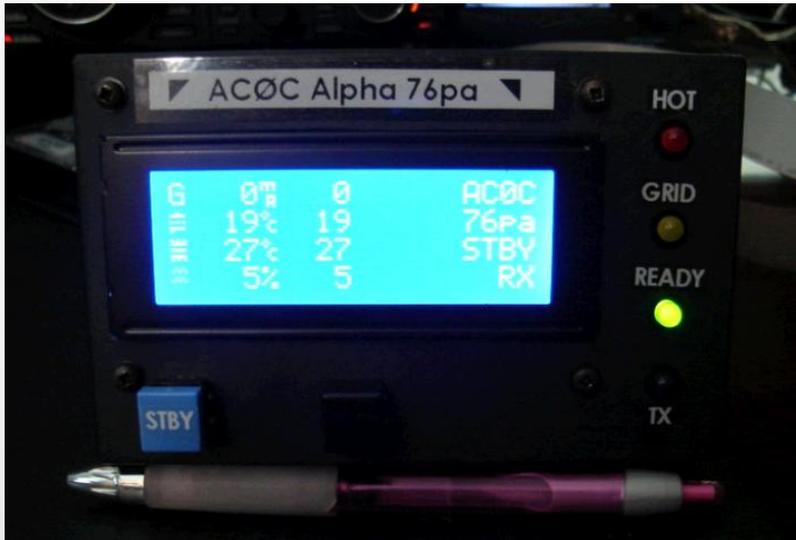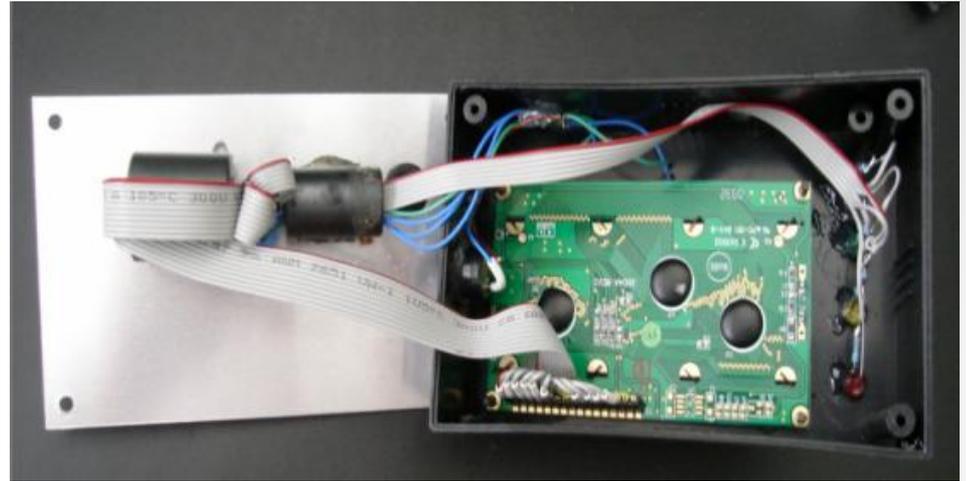

Amp + Control Head Shack Layout





Remaining Tasks

- Replace TV doorknobs with proper RF type
- Paint the not so beautiful pink relay foam
- LED mount – convert from breadboard to PCB
- Intermittent RCA jack on PTT line
- Faster grid protection trigger with 200W input slam

Lessons Learned

- 120V blows up parts very well!!!

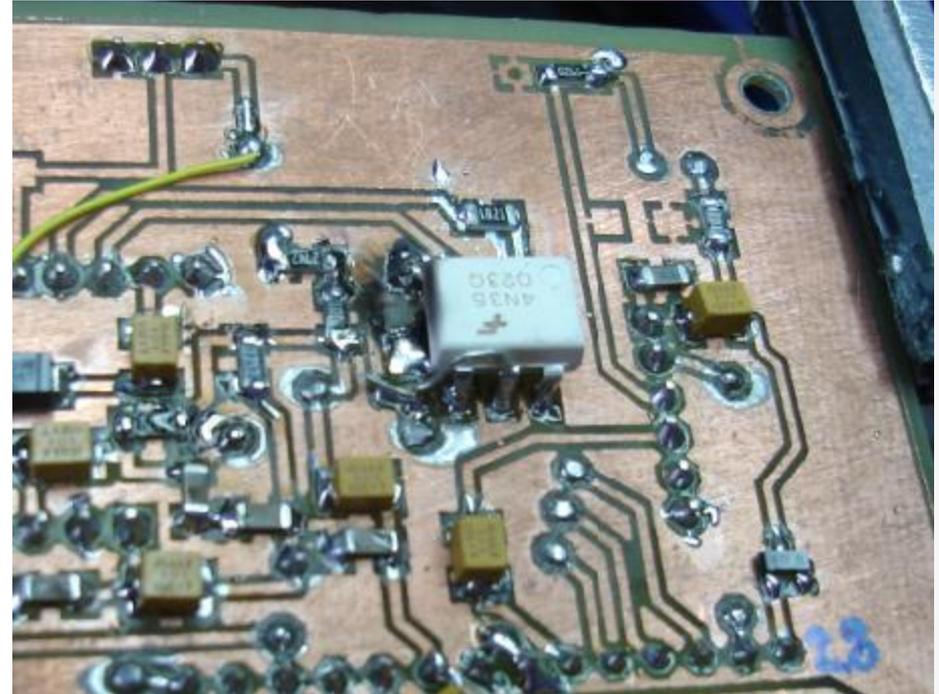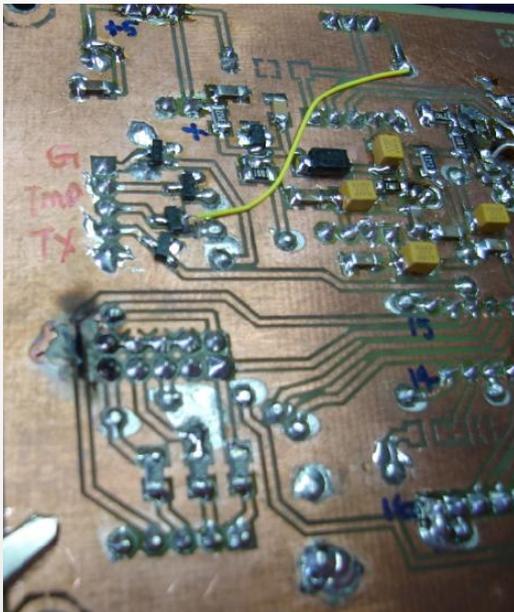

Special Thanks To:

- Lew Ward, K0LW
- Charlie Matzoch, W5VJN
- Rob Underwood, K0RU
- Matt Erickson, KK5DR
- Bob Wolbert, K6XX